

Digital Logic Design (EE1005)

Sessional-I Exam

Course Instructor(s):

Mr. Junaid Ali Khan, Ms. Naveen Khan, Ms.
Laraib Afzal, Ms. Samia Aziz, Ms. Maryam
Sana

Total Time (Hrs): 1

Total Marks: 40

Total Questions: 5

Date: Feb 23, 2026

Section(s): SE (A, B, C), CY (A,B,C), DS
(A,B), AI (A,B,C)

Roll No

Course Section

Student Signature

Do not write below this line.

Attempt all the questions.

1. *Calculator is allowed during the exam.*
2. *All steps must be shown clearly. Direct answers or missing steps will receive zero marks even if the final answer is correct.*
3. *Write all final answers clearly in the provided answer space. Only clean and clearly written solutions will be considered for marking.*
4. *Use the extra sheet for the rough. Answers written in the rough area will not be marked.*
5. *Attempt all questions neatly and label expressions, circuits and steps properly to receive full marks.*
6. *Any form of cheating or unauthorized assistance will result in cancellation of the paper.*
7. *Over writing, cutting and use of pencil will lead to zero marks*
8. *Rules/laws of boolean algebra are given at end page*
9. *Attempt Q4 and Q5 on answer sheet*

Attempt all the questions.

[CLO 1: Understand the foundations of digital logic, number systems and basic circuit concepts]

Q1: Convert the 8-bit gray code to its equivalent BCD (Binary-Coded Decimal) representation.
[5 marks]

11010110

National University of Computer and Emerging Sciences
Islamabad Campus

Sol

11010110

Gray → Binary:

Binary: 10011011

Binary → Decimal:

10011011 = 128+16+8+2+1

Decimal: 155

Decimal → BCD

BCD: 0001 0101 0101

Q2: Perform the addition of given numbers using BCD.


[5 Marks]



$$\begin{array}{r} \overset{1}{2} \quad \overset{1}{4} \quad \overset{1}{8} \quad 6 \\ + 3 \quad 6 \quad 9 \quad 7 \\ \hline 0110 \quad 1011 \quad 10010 \quad 1101 \\ \quad \quad 0110 \quad 0110 \quad 0110 \\ \hline 0110 \quad 0001 \quad 1000 \quad 0011 \end{array}$$

Q3: Convert the given AOI circuit into an equivalent circuit using only NOR gates. Simplify the circuit and redraw the final NOR-only implementation.

(Show all conversion steps clearly)

[4+4+2=10 marks]

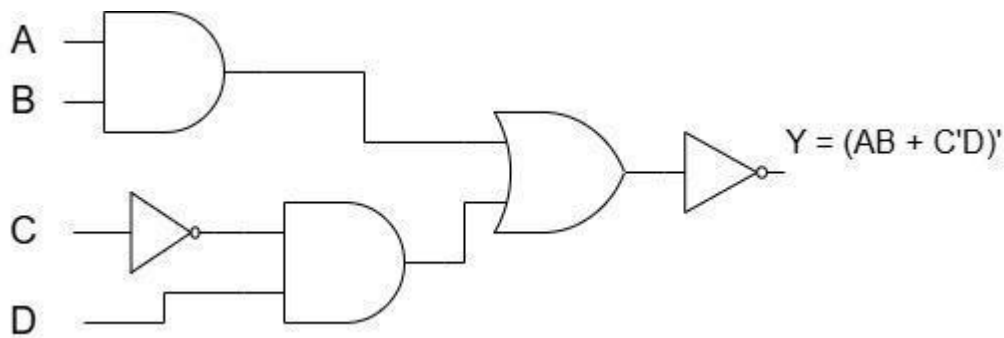

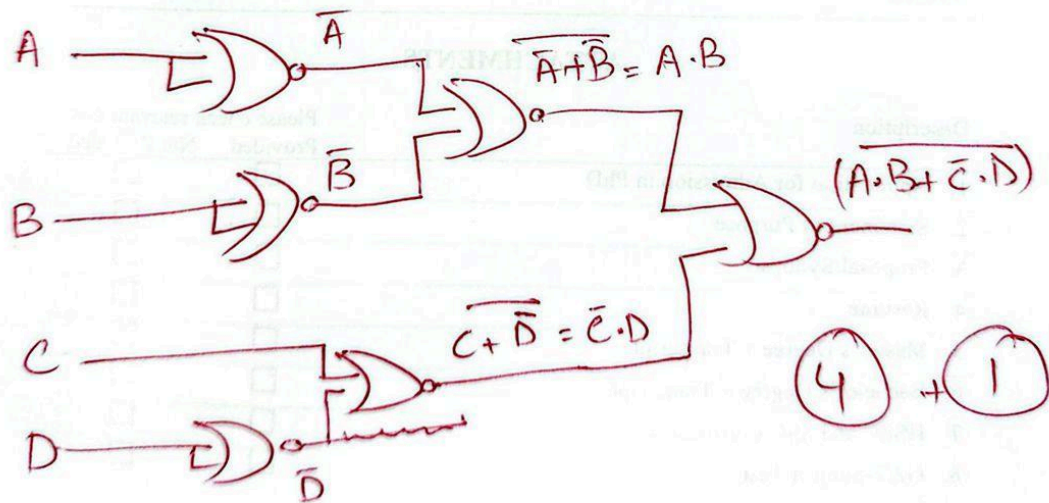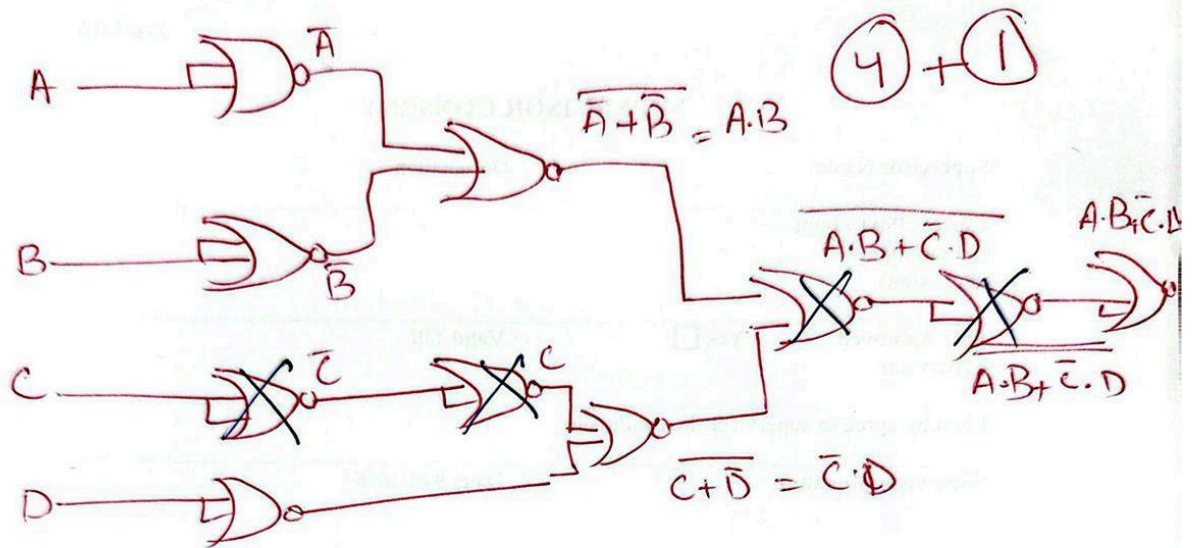

CS Scanned with CamScanner

Attempt Q4 and Q5 on answer sheet

[CLO 2: Demonstrate the acquired knowledge to apply techniques related to the design and

National University of Computer and Emerging Sciences

Islamabad Campus

analysis of digital electronic circuits including boolean algebra and multi variable karnaugh map methods(2)(3)]


Q4: Convert the given Boolean function into its standard form (Canonical Sum of Product). Derive the final equation, make a truth table and write the minterms like (m0,m1...) in it. [4+3=7marks]

$$F(A, B, C) = AB + BC + AC$$

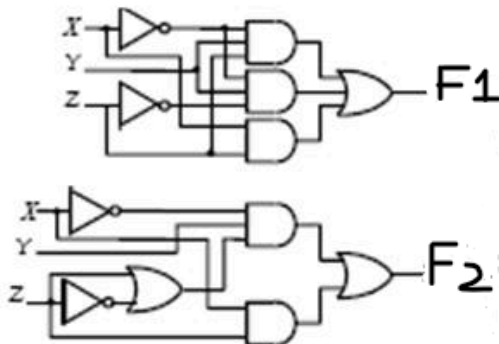Q5: Perform the analysis of the given circuit below

[4+2+3+4=13 Marks]

- Find Boolean expressions for **F1 and F2**.
- You must Simplify both(F1 and F2) Boolean expressions using Boolean algebra rules.
- Make sure to verify via the truth table(**F1=F2=simplified expression**).
- Redraw the circuit for **simplified expression** using **NAND** gate only.



Algebraic Rules/laws

National University of Computer and Emerging Sciences
Islamabad Campus

Postulate 2	(a)	$x + 0 = x$	(b)	$x \cdot 1 = x$
Postulate 5	(a)	$x + x' = 1$	(b)	$x \cdot x' = 0$
Theorem 1	(a)	$x + x = x$	(b)	$x \cdot x = x$
Theorem 2	(a)	$x + 1 = 1$	(b)	$x \cdot 0 = 0$
Theorem 3, involution		$(x')' = x$		
Postulate 3, commutative	(a)	$x + y = y + x$	(b)	$xy = yx$
Theorem 4, associative	(a)	$x + (y + z) = (x + y) + z$	(b)	$x(yz) = (xy)z$
Postulate 4, distributive	(a)	$x(y + z) = xy + xz$	(b)	$x + yz = (x + y)(x + z)$
Theorem 5, DeMorgan	(a)	$(x + y)' = x'y'$	(b)	$(xy)' = x' + y'$
Theorem 6, absorption	(a)	$x + xy = x$	(b)	$x(x + y) = x$